

# Project PREH

## Bazul 0

-  $S_1$  deschis

-  $i_{L0} = 0$ ,  $u_{C0} = 0$

$$\rightarrow i_{Lst} = 0,3 \text{ A}, u_{Cst} = 3 \text{ V}$$

## Bazul 1

-  $S_1$  închis

-  $i_{L0} = 0,3 \text{ A}$ ,  $u_{C0} = 3 \text{ V}$

• După o secundă  $u_{Cst} = 0 \text{ V}$ ,  $i_{Lst} = \infty$

•  $V = 0$  (absorbția)

•  $t_r = 3 \cdot R \cdot C = 30 \mu\text{s}$  (timpul de rădărire)

• De pe scapă  $t_r \approx 20 \mu\text{s}$

## Bazul 2

-  $S_1$  deschis

-  $i_{L0} = 0,6 \text{ A}$ ,  $u_{C0} = 1 \text{ V}$  (Bazul 1 pentru  $t_1 = 0,11 \mu\text{s}$ )

• După o secundă  $u_{Cst} = 3 \text{ V}$ ,  $i_{Lst} = 0,3 \text{ A}$

$$\cdot V = \frac{u_{Cmax} - u_{Cst}}{u_{Cst}} = \frac{3,335 - 3}{3} = 0,116 \rightarrow V = 11,6\%$$

• De pe scapă  $t_r \approx 6 \mu\text{s}$

## Bazul 3


- PWM

-  $i_{L0} = 0 \text{ V}$ ,  $u_{C0} = 0 \text{ V}$

•  $V = 0$

•  $t_r$

$S_1$  open

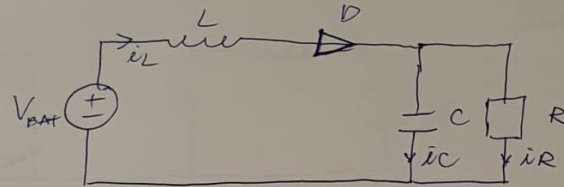

$$i_C = C \cdot \frac{d u_C}{dt}$$

$$u_L = L \cdot \frac{d i_L}{dt}$$


$$i_L = i_C + i_R$$

$$i_L = i_D$$

$$u_D = 0$$

$$V_{BAT} = u_L + u_D + u_C$$

$S_2$  closed

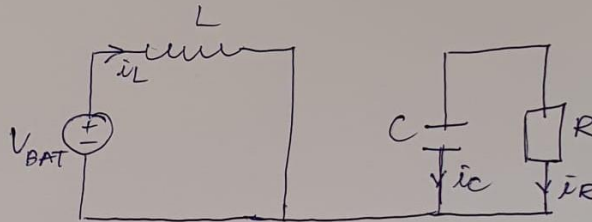


$$V_{BAT} = L \cdot \frac{d i}{dt}$$


$$i_D = 0$$

$$i_C = -i_R$$


## Simulink diagram for S1 open.

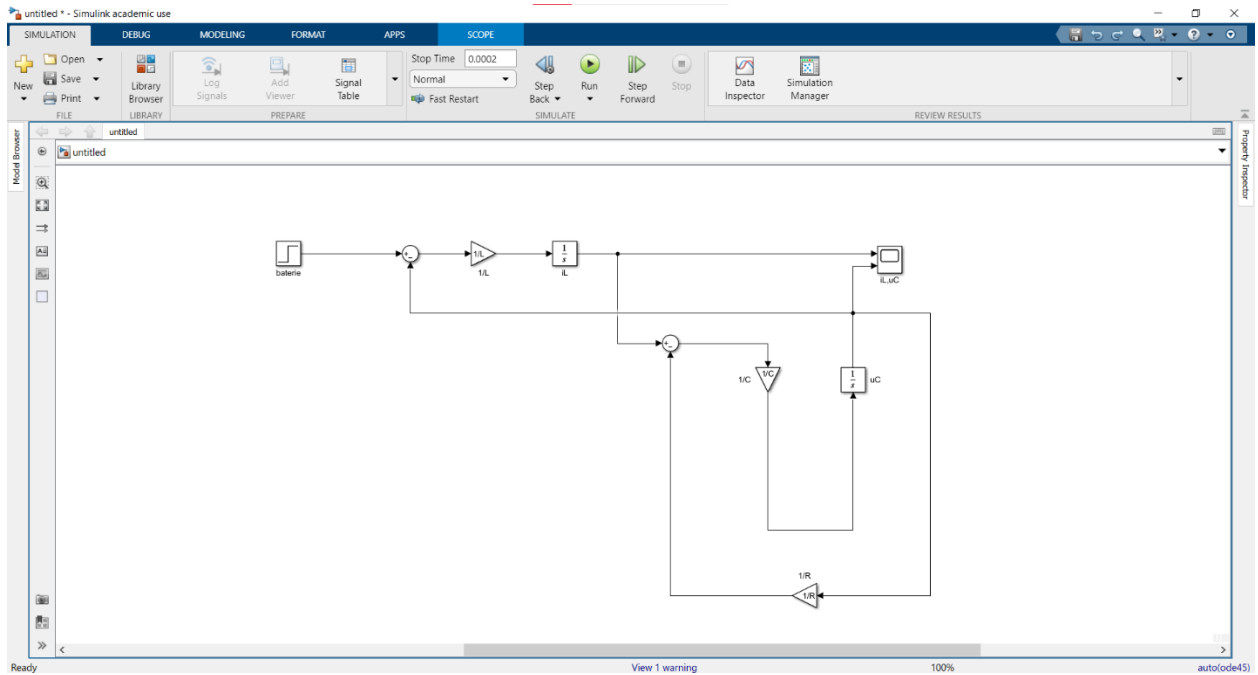

## Simulink diagram for S1 closed.

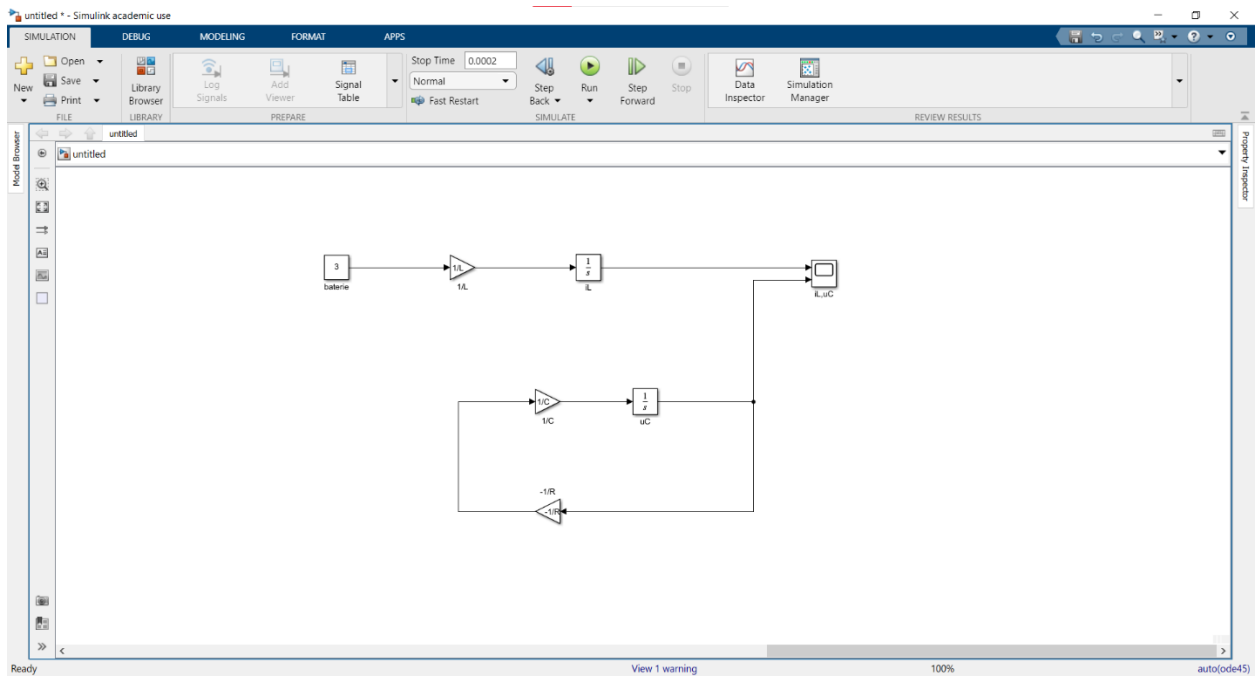

## Simulink diagram for PWM.

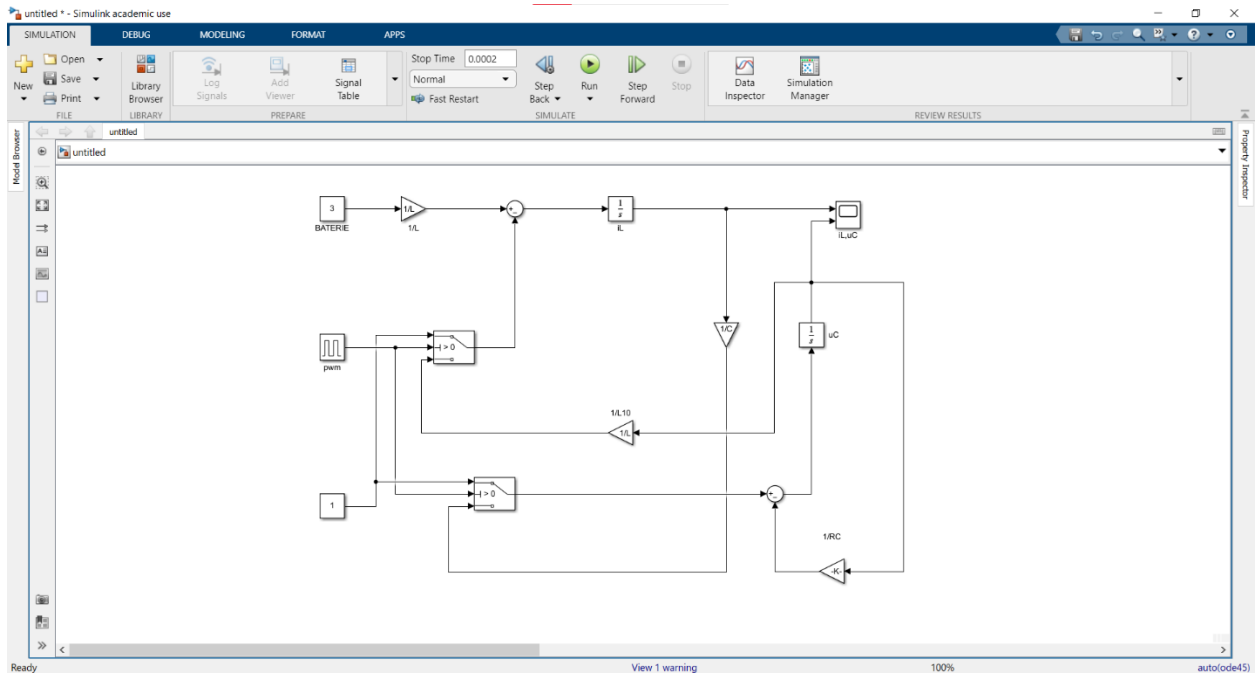

### 2.2.2.0)


Before we start with point 2.2.2.1, we need to have set initial conditions for differential equations for inductor and capacitor. I suppose the switch S1 is open in first place and I let 1 second for  $i_L$  and  $u_C$  to stabilize.



So the initial values for first exercise are  $i_{L0}=0.3[\text{A}]$  and  $u_{C0}=3[\text{V}]$ .
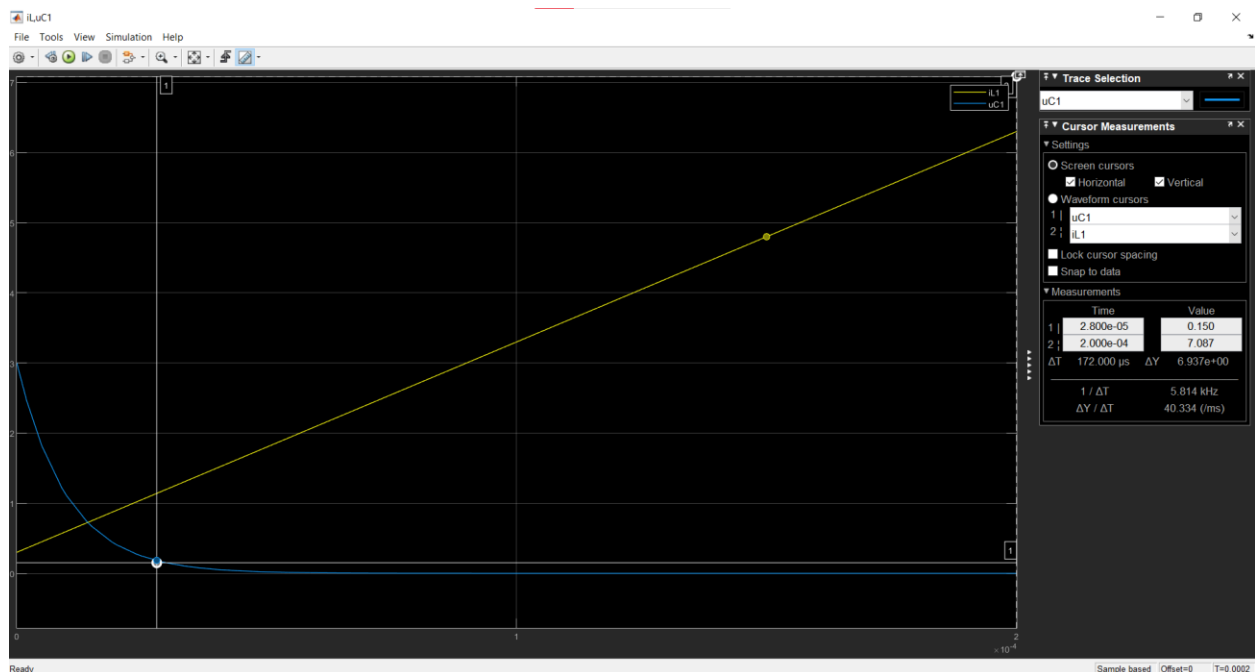
## 2.2.2.1)

S1 changes its state from open to closed.




In case of  $u_C$ , the system is stable and the steady-state value is  $0[V]$ , because capacitor discharges. After  $2\text{ ms}$  the value of  $u_C$  is  $0[V]$ , that means after  $1\text{ s}$  will be the same. The overshoot is also  $0$  and transient time(response time) is  $28\mu\text{s}$ .

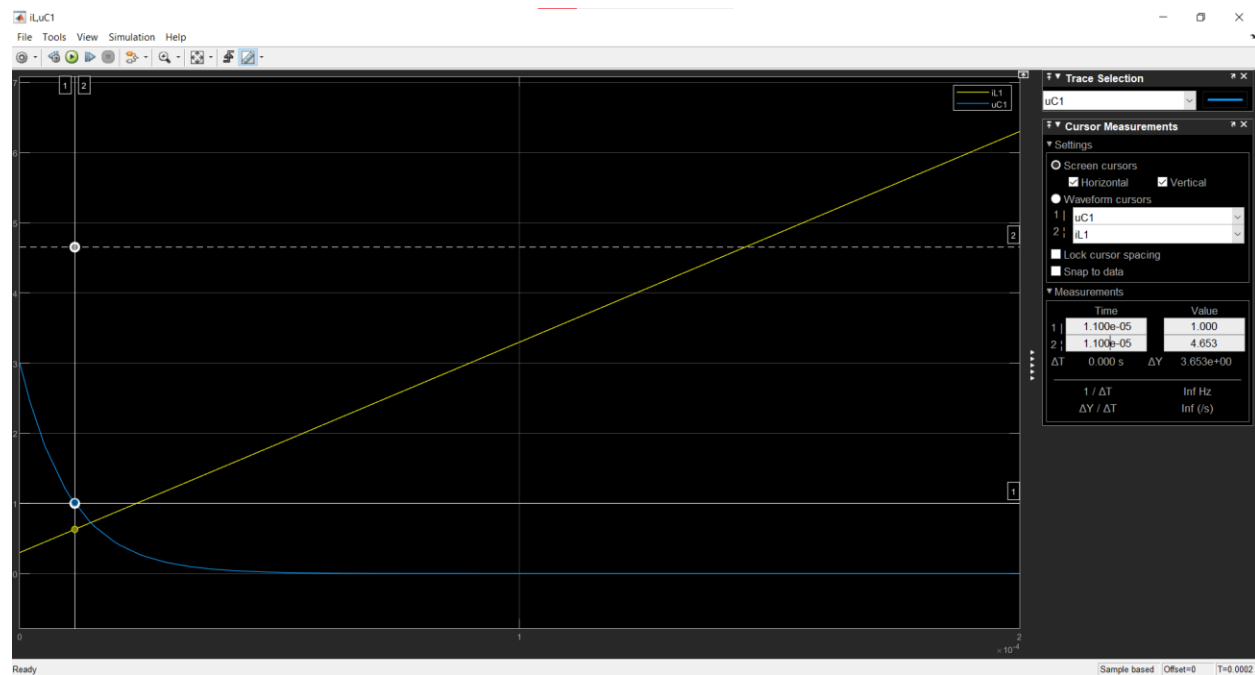
## 2.2.2.2)

$S_1$  changes its state from closed to open.

Again, we do not have initial values so I choose  $i_{L0}$  and  $u_{C0}$  after letting  $S_1$  closed for  $11\mu\text{s}$ . We have  $i_{L0}=0.6[A]$  and  $u_{C0}=1[V]$ .



Here I choose the peak value:

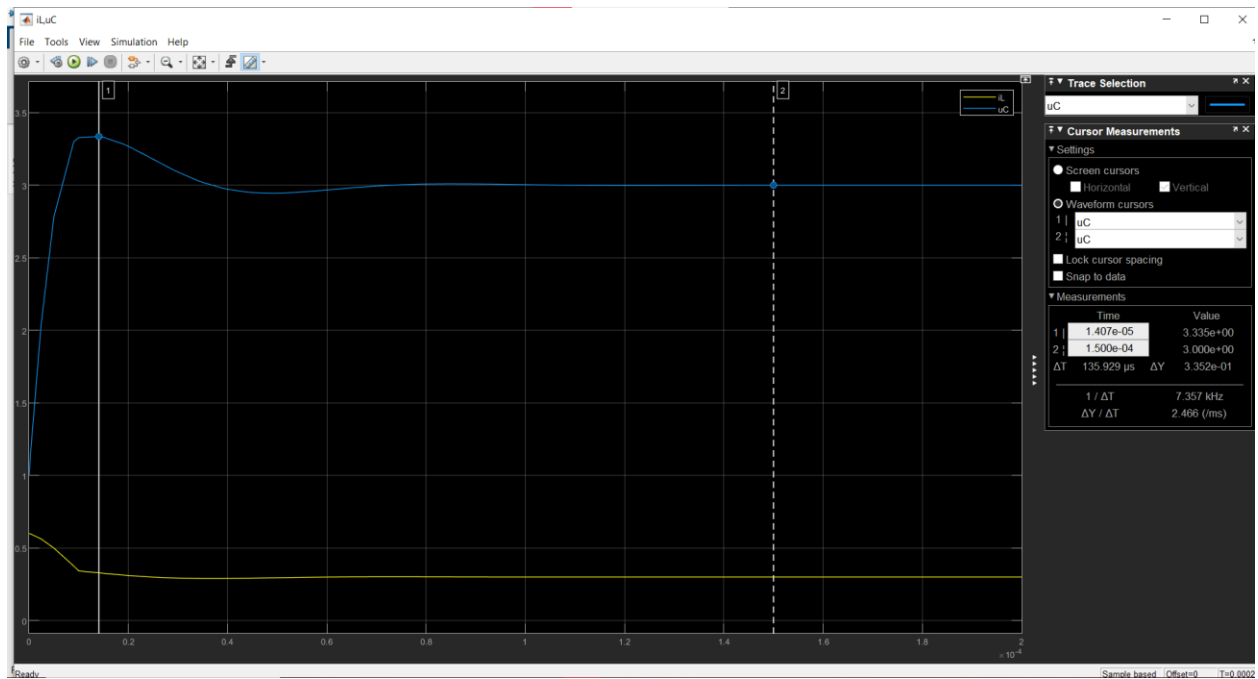


The system is stable again, because steady-state value of  $u_C$  is 3[V]. Value of  $u_C$  after 1s is also 3[V]. The overshoot is going to be 11,16% and the transient time will be 6 $\mu s$ .



### 2.2.2.3)

S1 is controlled by a PWM signal.

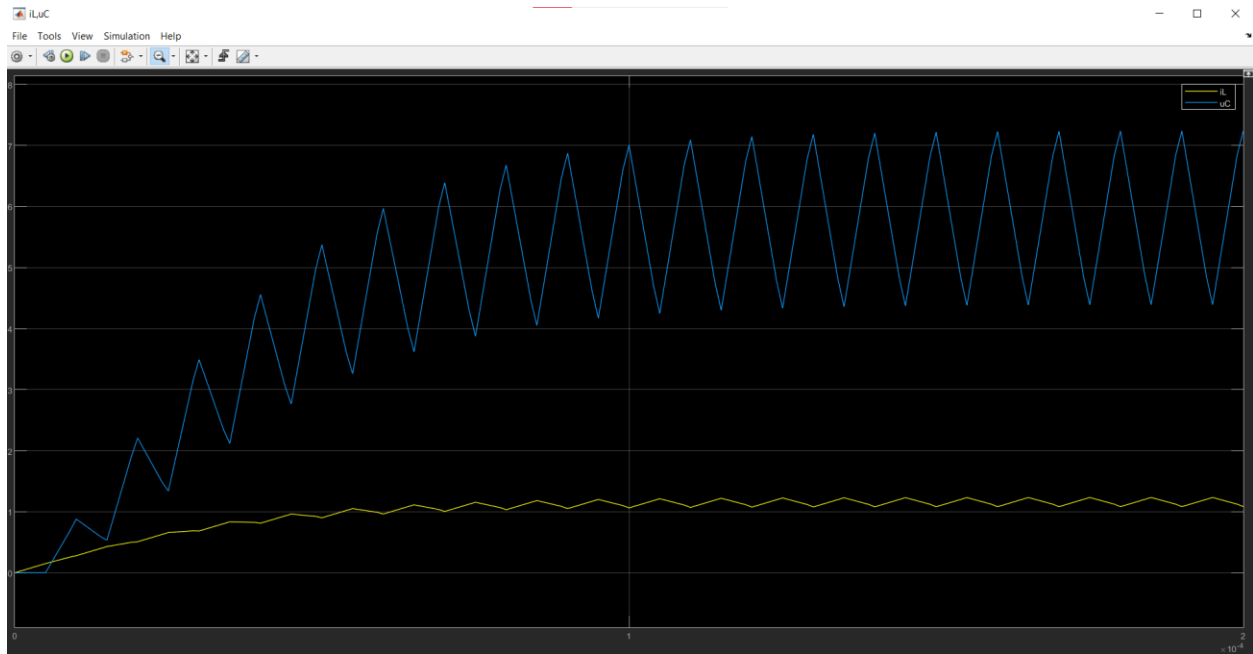

The system is marginally stable. Value of  $u_C$  is oscillating and the mean is 6[V] after 1s. Overshoot value and transient time value do not exist.